

**Instructions:-**

- (i) The marks are indicated in the right-hand margin.
- (ii) There are NINE questions in this paper.
- (iii) Attempt FIVE questions in all.
- (iv) Question No. 1 is compulsory.

- Q.1 Choose the correct answer of the following (Any seven question only):** **[2 x 7 = 14]**
- (a) For a base current of  $10\mu\text{A}$ , what is the value of collector current in common emitter if  $\beta_{dc} = 100$ ?
    - (i)  $10\mu\text{A}$
    - (ii)  $100\mu\text{A}$
    - (iii)  $1\text{mA}$
    - (iv)  $10\text{mA}$
  - (b) If an amplifier with gain of  $-1000$  and feedback factor  $\beta = -0.1$  had a gain change of  $20\%$  due to temperature, the change in gain of the feedback amplifier would be
    - (i)  $10\%$
    - (ii)  $5\%$
    - (iii)  $0.2\%$
    - (iv)  $0.01\%$
  - (c) A trivalent impurity has ..... Valence electrons.
    - (i) 4
    - (ii) 5
    - (iii) 6
    - (iv) 3
  - (d) Zener diodes are used primarily as .....
    - (i) Amplifiers
    - (ii) Voltage regulators
    - (iii) Rectifiers
    - (iv) Oscillators
  - (e) Peak inverse voltage of diode used in Half-wave rectifier is
    - (i)  $2V_m$
    - (ii)  $V_m/2$
    - (iii)  $V_m$
    - (iv)  $V_m/3$
  - (f) For every  $10^\circ\text{C}$  increase in temperature, the reverse saturation current of a p-n junction will be increased by:
    - (i) 10 times
    - (ii) 2 times
    - (iii) 4 times
    - (iv) Remain same
  - (g) A BJT transistor operates in which region when the base-emitter junction is forward-biased and the base-collector junction is reverse-biased?
    - (i) Active region
    - (ii) Saturation region
    - (iii) Cutoff region
    - (iv) Reverse active region
  - (h) In an RC phase shift oscillator, the phase shift provided by each RC stage is :
    - (i) 30 degree
    - (ii) 45 degree
    - (iii) 60 degree
    - (iv) 90 degree
  - (i) If the PIV rating of a diode is exceeded
    - (i) the diode conducts poorly
    - (ii) the diode is destroyed
    - (iii) the diode behaves as Zener diode
    - (iv) None of the above
  - (j) For  $I_{D05} = 9\text{mA}$  and  $V_p = -3.5\text{V}$ ,  $I_D$  for  $V_{GS} = 0\text{V}$  is
    - (i)  $8\text{mA}$
    - (ii)  $9\text{mA}$
    - (iii)  $10\text{mA}$
    - (iv)  $11\text{mA}$

- Q.2 (a) Define the following:**
- (i) Common mode rejection ratio (CMRR)
  - (ii) Gain bandwidth product
  - (iii) Slew rate of op-amp

- (b) State the Barkhausen condition for an electronic system to oscillate with feedback. [7]
- Q.3 (a) Derive the expression for stability factor for fix bias circuit with respect to  $I_{CO}$ ,  $V_{BE}$  and  $\beta$ . [7]
- (b) A voltage divider biased circuit has  $R_1=39k\Omega$ ,  $R_2=82k\Omega$ ,  $R_C=3.3k\Omega$ ,  $R_E=1k\Omega$  and  $CC=18V$ . The silicon transistor has used  $\beta = 120$ . Find Q - point and stability factor. [7]
- Q.4 (a) With the help of block diagram, explain the concept of feedback. [7]
- (b) Discuss with the help of circuit example, the purpose of providing - [7]
- (i) negative feedback;
- (ii) positive feedback in amplifier.
- Q.5 (a) With a neat circuit diagram and waveforms, explain the working of full wave bridge rectifier and show that its ripple factor is 0.48. [7]
- (b) Describe in detail the avalanche and Zener breakdown mechanism in Zener diode. [7]
- Q.6 (a) Derive the expression for output voltage of an instrumentation amplifier. Also write its advantages and disadvantages [8]
- (b) For an N-channel MOSFET the parameters given as  $\mu C_{ox} \frac{w}{L} = \frac{0.2mA}{V^2}$ ,  $V_{DS} = 0.2V$ , and  $V_i = 0.7V$ . Find the region of operation and the drain current. [6]
- Q.7 (a) Differentiate between JFET and BJT indicating the advantages and disadvantages. [7]
- (b) What is faithful amplification? Explain the conditions to be fulfilled to achieve faithful amplification in transistor amplifier. [7]
- Q.8 (a) Draw and explain the pin configuration of a 741 Op-Amp. Also explain the internal structure of an Op-Amp with the help of block diagram. [7]
- (b) For the circuit shown below. Assume zener voltage to be 4.78v and voltage drop across the forward biased zener to be 0.7v. Find the peak voltage of output. [7]
- Q.9 (a) State the characteristics of an ideal transformer. [2]
- (b) Define rms value, form factor, peak factor, complex power and half power frequency. [5]
- (c) Two two-port network a and b, with open-circuit impedances  $Z_a$  and  $Z_b$  are connected in series. Drive the Z-parameter equations. [7]



Circuit of Question No. 8(b)

