

Bihar Engineering University, Patna
End Semester Examination - 2022

Course: B.Tech.
Code: 100305

Semester: III
Subject: Digital Electronics

Time: 03 Hours
Full Marks: 70

Instructions:-

- (i) The marks are indicated in the right-hand margin.
- (ii) There are **NINE** questions in this paper.
- (iii) Attempt **FIVE** questions in all.
- (iv) Question No. 1 is compulsory.

Q.1 Choose the correct option of the following: (Answer any seven)

[2 x 7 = 14]

- (a) Dynamic RAM employs
 - (i) Capacitor or MOSFET
 - (ii) FET or JFET
 - (iii) Capacitor or BJT
 - (iv) BJT or MOS

- (b) The resolution of a 10-bit AD converter for an input range of 10 V is approximately
 - (i) 1 V
 - (ii) 1 mV
 - (iii) 10 mV
 - (iv) 100 mV

- (c) The parameter through which 16 distinct values can be represented is known as
 - (i) bit
 - (ii) byte
 - (iii) word
 - (iv) nibble

- (d) If we record any music in any recorder, such type of process is called
 - (i) Multiplexing
 - (ii) Encoding
 - (iii) Decoding
 - (iv) Demultiplexing

- (e) The systematic reduction of logic circuits is accomplished by
 - (i) Symbolic reduction
 - (ii) TTL logic
 - (iii) Boolean algebra
 - (iv) Truth table

- (f) In which of the following base system, 123 is not a valid number?
 - (i) BASE 10
 - (ii) BASE 16
 - (iii) BASE 8
 - (iv) BASE 3

- (g) A hexadecimal odometer displays F52F. The next reading will be
 - (i) F52E
 - (ii) G52F
 - (iii) F52F
 - (iv) F530

- (h) Sequential circuit contains;
 - (i) No memory element
 - (ii) All input applied simultaneously
 - (iii) At least one memory element
 - (iv) None

- (i) How many entries will be in the truth table of a 4-input NAND gate.
 - (i) 6
 - (ii) 8
 - (iii) 32
 - (iv) 16


- (j) Which ADC architecture is based on the principle of integrating an unknown input voltage over a fixed period of time?
 - (i) Flash ADC
 - (ii) Successive Approximation ADC
 - (iii) Dual slope ADC
 - (iv) Sigma-Delta ADC

- Q.2 (a) What are weighted, non-weighted, cyclic and self-complementary codes? Explain each with examples. [7]
- (b) Find the values of X in the following conversions: [7]
- $(95 \cdot 10)_{10}$ to $(X)_2$
 - $(45 \cdot 70)_8$ to $(X)_2$
 - $(168 \cdot 16)_8$ to $(X)_{16}$

- Q.3 (a) Design a BCD to 7-segment display decoder circuit using logic gates. [7]
- (b) Design full adder using the following: [7]
- 8:1 mux
 - 4:1 mux

- Q.4 (a) Define resolution, linearity, accuracy and settling time of D/A converters. A typical D/A converter has a full-scale analog output of 10 v and accepts 6 binary bits as input. What will be the voltage corresponding to each analog step? [7]
- (b) Design a 3-bit parallel comparator A/D converter that provides output in 2's complement format. [7]

 - Q.5 (a) Identify the following logic functions implemented at F: [7]



- (b) Implement the following CMOS logics: [7]
- $\overline{AB(A+B)}$
 - $\overline{((CD)+B)A}$

- Q.6 (a) What is binary shift register? Write down their application. [7]
- (b) Describe about Johnson ring counter using four D-flip-flop. [7]

- Q.7 (a) Minimize the following expression using k-map [7]
- $$f(P, Q, R, S) = \sum m(0, 1, 4, 5, 7, 12, 13)$$
- (b) Draw symbol and write the truth table of JK flip flop. [7]

- Q.8 (a) Describe the procedure to design Mod-6 counter. [7]
- (b) Explain SIPO and SISO operations of shift register with relevant logic diagrams and truth tables. [7]

- Q.9 Write short notes of the following [3.5x4]
- RAM
 - ROM
 - CMOS logic
 - Operation of TTL logic circuit working as NAND Gate