

Bihar Engineering University, Patna
End Semester Examination - 2022

Course: B.Tech.
Code: 100306

Semester: III
Subject: Electrical Circuit Analysis

Time: 03 Hours
Full Marks: 70

Instructions:-

- (i) The marks are indicated in the right-hand margin.
- (ii) There are **NINE** questions in this paper.
- (iii) Attempt **FIVE** questions in all.
- (iv) Question No. 1 is compulsory.

- Q.1 Choose the correct answer of the following (Any seven question only):** [2 x 7 = 14]
- (a) A 10 mH inductor carries a sinusoidal current of 1 A r.m.s at a frequency of 50 Hz. The average power dissipated by the inductor is
(i) 0 W (ii) 0.25 W (iii) 0.5 W (iv) 1.0 W
 - (b) Thevenin's equivalent circuit consists of
(i) current source and series impedance (ii) voltage source and series impedance
(iii) voltage source and shunt impedance (iv) current source and shunt impedance
 - (c) When the two quantities are in quadrature, the phase angle between them will be.
(i) 45° (ii) 90° (iii) 135° (iv) 60°
 - (d) A two-port network is symmetrical if
(i) $Z_{11}Z_{22} - Z_{12}Z_{21} = 1$ (ii) $AD - BC = 1$
(iii) $h_{11}h_{22} - h_{12}h_{21} = 1$ (iv) $Y_{11}Y_{22} - Y_{12}Y_{21} = 1$
 - (e) A two element series circuit is connected across an AC source given by
 $e = 200\sqrt{2}\sin(314t+20)V$
the current is found to be $i = 10\sqrt{2}\cos(314t-25)A$
the parameters of the circuit are
(i) $R = 20 \Omega$ and $C = 160\mu F$ (ii) $R = 14.14 \Omega$ and $C = 225\mu F$
(iii) $L = 45mH$ and $C = 225\mu F$ (iv) $L = 45mH$ and $C = 160\mu F$
 - (f) Superposition theorem is not applicable to networks containing
(i) nonlinear elements (ii) dependent voltage source
(iii) dependent current source (iv) transformers
 - (g) Which of the following is the Passive elements?
(i) Ideal current source (ii) Ideal voltage source
(iii) Capacitor (iv) All of these
 - (h) When a unit impulse voltage is applied to an inductor of 1 H, the energy supplied by the source is
(i) 2 J (ii) 1 J (iii) $\frac{1}{2}$ J (iv) $\frac{1}{4}$ J
 - (i) There are no transients in pure resistance circuits because they
(i) Offer high resistance (ii) obey Ohm's law
(iii) have no stored energy (iv) are linear circuits
 - (j) When a number of two-port network is cascaded, then
(i) Z-parameters are added up (ii) Y-parameters are added up
(iii) h-parameters are multiplied (iv) ABCD- parameters are multiplied

Q.2 Two mutually coupled identical coils are connected in series having self-inductance $L=4$ mH and mutual inductance $M=2$ mH.


- (a) What are the maximum and minimum possible values of equivalent inductances?
- (b) Determine the coefficient of coupling between the coils.

- Pr. Q.3/ (a) Prove that the average power in an AC circuit is given by $W = VI \cos \phi$, where symbols have their usual meanings. [6]
- (b) A voltage of $e(t) = 150 \sin 1000t$ is applied across a series R-L-C circuit, where $R = 40 \Omega$, $L = 0.13 \text{ H}$ and $C = 10 \mu\text{F}$. [8]
- Compute the r.m.s value of the steady-state current
 - Find the r.m.s voltage across the inductor.
 - Find the r.m.s voltage across the capacitor
 - Determine the active and reactive power supplied by the source.

- Q.4/ (a) Find the Laplace transform of $f(t) = e^{-at} \cos(0t)$, $a > 0$. [4]
- (b) Calculate the inverse Laplace transform of $F(s) = \frac{1}{s(s^2 - a^2)}$ [5]
- (c) In the series R-C circuit, the capacitor has an initial charge 2.5 mC . At $t=0$, the switch is closed and a constant voltage source $V = 100 \text{ V}$ is applied. Use the Laplace transform method to find the current in the circuit after closing the switch. [5]


- Q.5 (a) Two impedances $Z_1 = 40 \angle 30^\circ \Omega$ and $Z_2 = 30 \angle 60^\circ \Omega$ are connected in series across a single-phase 230 V , 50 Hz supply. Calculate the [7]
- Current drawn
 - pf, and
 - power consumed by the circuit.
- (b) State and explain the Super Position Theorem and find out the step to be followed in super position theorem. [7]

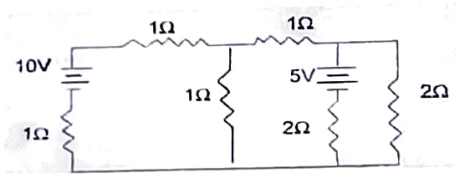- Q.6/ (a) State maximum power transfer theorem. Prove that efficiency of the circuit under maximum power transfer condition is 50%. [7]
- (b) Draw the Thevenin equivalent circuit of the figure shown below and hence find the current through $R=2\Omega$. [7]



$I = \frac{V}{R}$

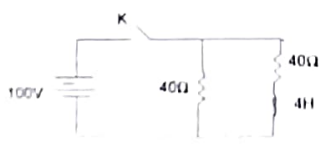- Q.7 (a) Find the current in a series RL circuit having $R = 2 \Omega$ and $L = 10 \text{ H}$ while a d.c voltage of 100 V is applied. What is the value of this current after 5 secs of switching on? [7]
- (b) In given fig. A steady state condition is reached with 100 V d.c source At $t=0$, switch K is suddenly open. Find the expression of current through the inductor after $t=0.5 \text{ sec}$. [7]



$I = \frac{V}{R} = \frac{100}{40} = 2.5 \text{ A}$

$V = IR$

Handwritten notes on the left margin: $20, 1500, 90, 80, 80, 100, 20$

- Q.8 (a) Define apparent power and Reactive power. [4]
- (b) The current in a circuit lag the voltage by 30° if the power be 400 W and the supply voltage be $v = 100 \sin(377t + 10^\circ)$ find complex power [5]
- (c) In an ac circuit $v = 100 \sin(\omega t + 30^\circ) \text{ V}$, $i = 5 \sin(\omega t - 30^\circ) \text{ A}$. find apparent power, real power and reactive power. [5]

- Q.9 Write short notes on the following: [3.5x4=14]
- Reciprocity Theorem
 - Laplace Theorem
 - Two port network
 - Resonance